


# **GATE**

---

# **2018**

**ELECTRICAL AND  
ELECTRONIC  
MEASUREMENT**

**ELECTRICAL ENGINEERING**

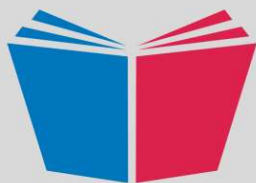

**ECG**  
Publications



A Unit of **ENGINEERS CAREER GROUP**

**Head Office:** S.C.O-80-81-82, 3<sup>rd</sup> floor, Sector-34/A, Chandigarh-160022

**Website:** [www.engineerscareergroup.in](http://www.engineerscareergroup.in)

**Toll Free:** 1800-270-4242

**E-Mail:** [ecgpublications@gmail.com](mailto:ecgpublications@gmail.com)

| [info@engineerscareergroup.in](mailto:info@engineerscareergroup.in)

**GATE-2018:** Electrical and Electronic Measurement | Detailed theory with GATE & ESE previous year papers and detailed solutions.

©Copyright @2016 by ECG Publications

*(A unit of ENGINEERS CAREER GROUP)*

All rights are reserved to reproduce the copy of this book in the form storage, introduced into a retrieval system, electronic, mechanical, photocopying, recording, screenshot or any other form without any prior written permission from ECG Publications (A Unit of ENGINEERS CAREER GROUP).

**First Edition:** 2016

**Price of Book:** INR 509/-

---

**ECG PUBLICATIONS** (A Unit of ENGINEERS CAREER GROUP) collected and proving data like: theory for different topics or previous year solutions very carefully while publishing this book. If in any case inaccuracy or printing error may find or occurred then **ECG PUBLICATIONS** (A Unit of ENGINEERS CAREER GROUP) owes no responsibility. The suggestions for inaccuracies or printing error will always be welcome by us.

# CONTENTS

CHAPTER	PAGE
1. MEASUREMENTS AND MEASUREMENT SYSTEMS.....	1-7
2. CHARACTERISTICS OF INSTRUMENTS AND MEASUREMENT SYSTEMS.....	8-29
3. ERRORS IN MEASUREMENTS AND THEIR STATISTICAL ANALYSIS.....	30-51
4. ANALOG INSTRUMENTS.....	52-76
5. ANALOG AMMETER, VOLTMETER AND OHMMETER... ..	77-119
6. MEASUREMENT OF POWER.....	120-163
7. MEASUREMENT OF RESISTANCE.....	164-189
8. AC BRIDGE.....	190-221
9. ELECTRONIC MEASUREMENTS.....	222-249
10. CATHODE RAY OSCILLOSCOPE .....	250-290
11. INSTRUMENT TRANSFORMERS.....	291-301
12. PRIMARY SENSING ELEMENTS AND TRANSDUCERS.....	302-364





**CHAPTER - 1*****MEASUREMENTS AND MEASUREMENT SYSTEMS*****1.1 MEASUREMENTS**

Measurement of quantity is result of comparison of the quantity under measurement, also called as measurand, with perfect standard. The result is expressed in numerical values.

There are two methods to measure:

**1. Direct Method**

The measurement is compared directly with the standard.

**Example.** Measurement of length by tape.

**2. Indirect Method**

The measurand is measured by use of measuring instruments.

**1.1.1 Measurement Instruments*****1. Mechanical Instruments***

They are good for static measurement i.e. measurand is not varying with time. Due to inertia, mechanical instruments are not suitable for dynamic measurement.

***2. Electrical Instruments***

They are better than mechanical instruments for dynamic measurements. However electrical systems use mechanical parts.

***3. Electronic Instruments***

Because the mass of electron is very less, the electronic systems are fastest.

In these, amplification of the signal can be done, hence very weak signals can also be measured.

**1.1.2 Properties**

1. Highest sensitivity
2. Power consumption is least
3. Most reliable
4. Fastest response
5. Low weight

**1.1.3 Classification of Instruments*****1. Absolute Instruments***

The magnitude of measurand is measured in terms of the instruments constants. For eg: Tangent Galvanometer, rayleigh current balance. They are used for calibrating secondary instruments.

***2. Secondary Instruments***

They are calibrated with absolute instruments. The measurand is observed by output indication.

***3. Deflection – Type Instruments***

The measurand produces force or torque for deflection. Opposing torque to this deflection is produced externally. At the point of balance,

Deflection torque = controlling torque.

## ESE OBJ QUESTIONS

1. A resistance of  $108 \Omega$  is specified using significant figures as indicated below:

1.  $108 \Omega$
2.  $108.0 \Omega$
3.  $0.00108 \Omega$

[EE ESE - 2011]

Among these:

- (a) 1 represents greater precision than 2 and 3.
- (b) 2 represent greater precision but 1 and 3 represents same precision.
- (c) 2 and 3 represent greater precision than 1
- (d) 1, 2 and 3 represents same precision

2. A resistance of 105 ohms is specified using significant figures as indicated below:

1. 105 ohms
2. 105.0 ohms
3.  $0.000105 \text{ M}\Omega$

[EE ESE - 2010]

Among these

- (a) 1 represents greater precision than 2 and 3.
- (b) 2 and 3 represent greater precision than 1.
- (c) 1, 2 and 3 represent same precision.
- (d) 2 represents greater precision but 1 and 3 represent same precision.

3. What is the prefix tera equivalent to?

- (a)  $10^3$
- (b)  $10^6$
- (c)  $10^9$
- (d)  $10^{12}$

[EE ESE - 2008]

4. For defining the standard meter, wavelength of which material is considered?

- (a) Neon
- (b) Krypton
- (c) Helium
- (d) Xenon

[EE ESE - 2006]

5. Which one of the following is the most stable frequency primary atomic standard for frequency

- (a) Caesium beam standard
- (b) Hydrogen maser standard

[EC ESE - 2005]

- (c) Rubidium vapour standard
- (d) Quartz crystal standard

6. Match List-I (Accuracy) with List-II (Type of the standard) and select the correct answer:

**List-I**

- A. Least accurate
- B. More accurate
- C. Much more accurate
- D. Highest possible accurate

**List-II**

- (i) Primary
- (ii) Secondary
- (iii) Working
- (iv) International

[EE ESE - 2004]

**Codes:**

- (a) A-iii, B-iv, C-i, D-ii
- (b) A-i, B-iv, C-iii, D-ii
- (c) A-iii, B-ii, C-i, D-iv
- (d) A-i, B-ii, C-iii, D-iv

7. For time and frequency, the working standard is

[EE ESE - 2003]

- (a) Microwave oscillator
- (b) Crystal controlled oscillator
- (c) Laser
- (d) ARF oscillator

8. The most suitable primary standard for frequency is

[EC ESE - 2002]

- (a) Rubidium vapour standard
- (b) Quartz standard
- (c) Hydrogen maser standard
- (d) Caesium beam standard

9. The modern standard of time

[EE ESE - 2001]

- (a) A second defined as  $1/86400$  of a mean solar day.

(b) A second defined as time constant of an RC series circuit having  $R = 2 \text{ M}\Omega$ ,  $C = 500 \text{ pF}$ .

(c) A second which is duration of 9192631770 periods of radiation corresponding to the transition between the two hyperfine levels of the fundamental state of the atom cesium 133.

(d) A second defined as  $1/31556925.9747$  of the time required by the earth to orbit the sun in the year 1900.

10. The resistivity of the wire material can be expressed in terms of LMTI system of dimensional parameter as

[EC ESE - 2001]

(a)  $\text{ML}^2\text{T}^{-2}\text{I}^{-2}$   
(c)  $\text{ML}^3\text{T}^{-3}\text{I}^{-2}$

(b)  $\text{ML}^2\text{T}^{-3}\text{I}^{-2}$   
(d)  $\text{ML}^3\text{T}^{-2}\text{I}^{-2}$

11. "The current internationally recognized unit of time and frequency is based on the cesium clock, which gives an accuracy better  $1 \mu\text{s}$  per day". This statement is related to

[EC ESE - 1999]

- (a) Working standards
- (b) International standards
- (c) Primary standards
- (d) Secondary standards

ENGINEERS CAREER GROUP

# SOLUTIONS

**Sol. 1. (b)**

1.  $108 \Omega$  has 3 significant figures.
  2.  $108.0 \Omega$  has 4 significant figures.
  3.  $0.000108 \text{ M}\Omega$  can be written has  $108 \Omega$ .
- So, it has 3 significant figures.

The more the significant figures, the greater the precision of measurement.

Hence, option (b) is correct.

**Sol. 2. (d)**

**Sol. 3. (d)**

**Sol. 4. (b)**

**Sol. 5. (b)**

The hydrogen maser is the most stable frequency source currently known, having a frequency of  $1420405751.73 \pm 0.03 \text{ Hz}$ . However, due to its relatively large size, its use is limited to area where stability is critical, and size is not a consideration

**Sol. 6. (c)**

**Sol. 7. (b)**

**Sol. 8. (d)**

**Sol. 9. (c)**

**Sol. 10. (c)**

$$R = \frac{\rho l}{A} \Rightarrow \rho = \frac{RA}{l}$$

$$\text{But } R = \frac{V}{i} \text{ where } V = \frac{W}{Q}$$

$$\text{So, } \rho = \frac{W}{Q} \cdot \frac{1}{i} \cdot \frac{A}{l}$$

Where

W = work

Q = charge

i = current

A = area

l = length

Considering dimensions

$$\rho = \frac{ML^2T^{-2}}{IT} \cdot \frac{1}{i} \cdot \frac{L^2}{L}$$


$$\text{Or } \rho = ML^3T^{-3}I^{-2}$$

So, the dimension of resistivity is  $ML^3T^{-3}I^{-2}$

**Sol. 11. (c)**

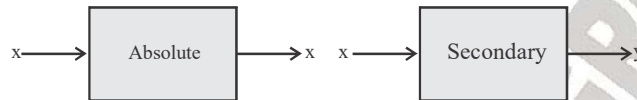**CHAPTER - 2****CHARACTERISTICS OF INSTRUMENTS AND MEASUREMENT SYSTEMS****2.1 STATIC CHARACTERISTICS****1. Calibration Curve**

In this process, a known quantity is given as an input to instrument and output is seen. If output varies then instrument is adjusted accordingly using absolute instruments.



Adjust instrument so that output is x

**2. Accuracy**

Conformity to truth, or true value. True value is impossible to calculate. However, most agreed value by experts may be considered as true value.

Measured in terms of its error.

Static error = Measured value – True value

$$\delta A = A_m - A_t$$

Absolute error/static error ( $\delta A$ ) =  $E_0 = A_m - A_t$

Relative error,

$$E_r = \frac{\delta A}{A_t}$$

**(i) Accuracy is specified in three ways****(a) Point Accuracy**

Only for a particular value the instrument is accurate to measure

(b) Accuracy as percentage of scale range i.e., x% of full scale deflection.

(c) Accuracy as percentage of true value i.e., x% of true value.

**3. Static Correction**

$$\delta C = -(\delta A)$$

Error is corrected in opposite to the error.

**4. Scale Range**

The range from minimum to maximum that instrument can measure.

**5. Scale Span**

$$X_{\max} - X_{\min} = \text{Scale Span}$$

**6. Reproducibility and Drift**

The degree of closeness with which a given value can be measured repeatedly at different times in reproducibility.

If there is perfect reproducibility over time that is called No Drift.

## GATE QUESTIONS

1. Two magnetically uncoupled inductive coils have Q factors  $q_1$  and  $q_2$  at the chosen operating frequency. Their respective resistances are  $R_1$  and  $R_2$ . When connected in series. Their effective Q factor at the same operating frequency is

[GATE - 2013]

- (a)  $q_1 + q_2$
- (b)  $(1/q_1) + (1/q_2)$
- (c)  $(q_1R_1 + q_2R_2)/(R_1 + R_2)$
- (d)  $(q_1R_2 + q_2R_1)/(R_1 + R_2)$

## SOLUTIONS

**Sol. 1. (c)**

The quality factor of the inductances are given by

$$q_1 = \frac{\omega L_1}{R_1} \text{ and } q_2 = \frac{\omega L_2}{R_2}$$

So, in series circuit, the effective quality factor is given by

$$Q = \frac{|X_{Leq}|}{R_{eq}} = \frac{\omega L_1 + \omega L_2}{R_1 + R_2}$$

$$= \frac{\frac{\omega L_1}{R_1} + \frac{\omega L_2}{R_2}}{\frac{1}{R_2} + \frac{1}{R_1}} = \frac{q_1 + q_2}{\frac{1}{R_2} + \frac{1}{R_1}} = \frac{q_1R_1 + q_2R_2}{R_1 + R_2}$$

**CHAPTER - 3*****ERRORS IN MEASUREMENTS AND THEIR STATISTICAL ANALYSIS*****3.1 INTRODUCTION****3.1.1 Limiting Errors/ Guarantee Errors**

Limiting error is the deviation from nominal value guaranteed by manufacturer.

$$A_a = A_s \pm \delta A$$

Where  $A_a$  is Actual value

$$\text{Relative limiting Error}(E_r) = \frac{\text{Actual Value} - \text{Nominal Value}}{\text{Nominal Value}} = \frac{\delta A}{A_s}$$

**Example** A wattmeter has fsd 1000W and error  $\pm 1\%$  fsd. What will be the range of value if we measure 100W if error was specified as percentage of true value.

**Solution.**

$$\text{Magnitude of limiting error at fsd} = \pm \frac{1}{100} \times 1000 = \pm 10W$$

$$\Rightarrow 100 \pm 10W \text{ i.e., Between } 90W \text{ to } 110W$$

$$\text{Percentage of } E_r = \pm \frac{10}{100} \times 100 = \pm 10\%$$

If error given as percentage of true value

$$\text{Magnitude} = \pm \frac{1}{100} \times 100 = \pm 1W$$

Hence, meter will read from 99 to 101 W

**Example** A 0 – 150V voltmeter has guaranteed accuracy of 1% of fsd. At = 75V. what is the limiting error ?

**Solution.**

$$\delta A = \frac{1}{100} \times 150 = 1.5$$

$$A_t = 75V$$

$$\text{Percentage of } E_r = \frac{1.5}{75} \times 100 = 2\%$$

**3.1.2 Limiting error of components/combination of quantities****1. Addition**


$$x = x_1 + x_2$$

$$\frac{dx}{x} = \pm \frac{d(x_1 + x_2)}{x}$$

$$\frac{dx}{x} = \pm \left[ \left( \frac{\partial x_1}{x_1} \cdot \frac{x_1}{x} \right) + \left( \frac{\partial x_2}{x_2} \cdot \frac{x_2}{x} \right) \right]$$

## GATE QUESTIONS

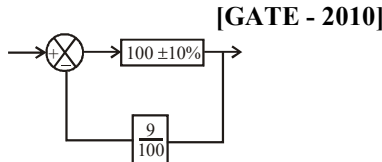1. As shown in the figure, a negative feedback system has an amplifier of gain 100 with + 10% tolerance in the forward path, and an attenuator of value 9/100 in the feedback path. The overall system gain is approximately



- (a)  $10 \pm 1\%$   
(c)  $10 \pm 5\%$

- (b)  $10 \pm 2\%$   
(d)  $10 \pm 10\%$

2. A variable  $w$  is related to three other variables  $x, y, z$  as  $w = xy/z$ . The variables are measured with meters of accuracy  $\pm 0.5\%$  reading,  $\pm 1\%$  of full scale value and  $\pm 1.5\%$  reading. The actual readings of the three meters are 80, 20 and 50 with 100 being the full scale value for all three. The maximum uncertainty in the measurement of  $w$  will be

[GATE - 2006]

- (a)  $\pm 0.5\%$  rdg      (b)  $\pm 5.5\%$  rdg  
(c)  $\pm 6.7\%$  rdg      (d)  $\pm 7.0\%$  rdg

## SOLUTIONS

**Sol. 1. (a)**

Overall gain of the system is

$$g = \frac{100}{1 + 100 \left( \frac{9}{100} \right)} = 10 \text{ (zero error)}$$

Gain with error

$$g = \frac{100 + 10\%}{1 + (100 + 10\%) \left( \frac{9}{100} \right)}$$

$$= \frac{110}{1 + \frac{110 \times 9}{100}} = 10.091$$

$$\text{error } \Delta g = 10.091 - 10 \approx 0.1$$

Similarly

$$g = \frac{100 - 10\%}{1 + (100 - 10\%) \frac{9}{100}} = \frac{90}{1 + 90 \times \frac{9}{100}} = 9.89$$

$$\text{Error } \Delta g = 9.89 - 10 \approx -0.1$$

$$\text{So gain } g = 10 \pm 0.1 = 10 \pm 1\%$$

**Sol. 2. (d)**

$$\text{Given that } \omega = \frac{xy}{z}$$

$$\log \omega = \log x + \log y - \log z$$

Maximum error in  $\omega$

$$\% \frac{d\omega}{\omega} = \pm \frac{dx}{x} \pm \frac{dy}{y} \pm \frac{dz}{z}$$

$$\frac{dx}{x} = \pm 0.5\% \text{ readings}$$

$$\frac{dy}{y} = \pm 1\% \text{ full scale} = \pm \frac{1}{100} \times 100 = \pm 1$$

$$\frac{dy}{y} = \pm \frac{1}{20} \times 100 = \pm 5\% \text{ reading}$$

$$\frac{dz}{z} = 1.5\% \text{ reading}$$

$$\text{So } \% \frac{d\omega}{\omega} = \pm 0.5\% \pm 5\% \pm 1.5\% = \pm 7\%$$




## CHAPTER - 4

### ANALOG INSTRUMENTS


#### 4.1 INTRODUCTION
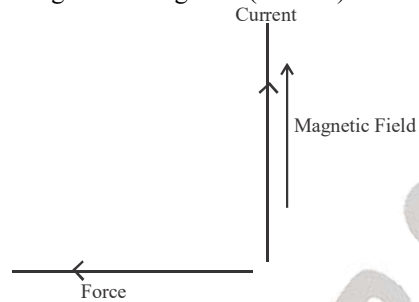
##### 4.1.1 Fleming's Left Hand Rule

This rule is used in Permanent Magnet Moving Coil (PMMC)



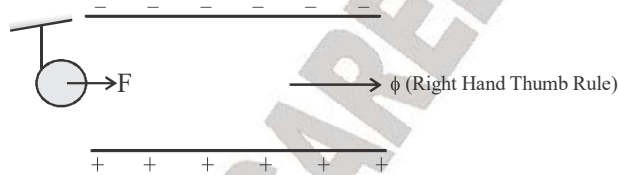When an iron piece is placed near magnetic field then magnetic energy acts in such a way so as to reduce reluctance.



$$\text{Reluctance} = \frac{\text{mmf}}{\text{flux}} = \frac{NI}{\phi}$$

Where mmf is Magneto Motive Force

emf is Electro Motive Force

##### 4.1.2 Ampere's Law

$$\oint H \cdot d\ell = I_{\text{enclosed}}$$

where H is Magnetic Field Intensity

$\oint$  is magnetic path enclosed

$$H \times \ell_m = NI$$

Where  $\ell_m$  is length of magnetic path

##### 4.1.3 Right Hand Thumb Rule

Thumb is the direction of current and curl of fingers is the direction of flux.

## GATE QUESTIONS


1. A current of  $-8+6\sqrt{2}(\sin \omega t + 30^\circ)$  A is passed through three meters. They are a centre zero PMMC meter, a true rms meter and a moving iron instrument. The respective reading (in A) will be

[GATE - 2006]

- (a) 8, 6, 10                      (b) 8, 6, 8  
(c) -8, 10, 10                    (d) -8, 2, 2

2. The set-up in the figure is used to measure resistance  $R$ . The ammeter and voltmeter resistances are  $0.01\Omega$  and  $2000\Omega$ , respectively. Their readings are 2 A and 180 V, respectively, giving a measured resistance of  $90\Omega$ . The percentage error in the measurement is

[GATE - 2005]

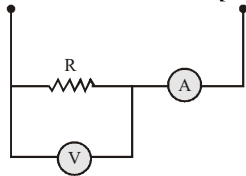

- (a) 2.25%                            (b) 2.35%  
(c) 4.5%                             (d) 4.71%

3. A moving coil of a meter has 100 turns, and a length and depth of 10 mm and 20 mm respectively. It is positioned in a uniform radial flux density of 200 mT. The coil carries a current of 50 mA. The torque on the coil is

[GATE - 2004]

- (a)  $200\mu\text{Nm}$                       (b)  $100\mu\text{Nm}$   
(c)  $2\mu\text{Nm}$                         (d)  $1\mu\text{Nm}$

4. A dc A-h meter is rated for 15 A, 250 V. The meter constant is 1.4,4 A-sec/rev. The meter constant at rated voltage may be expressed as


[GATE - 2004]

- (a) 3750 rev/kWh                  (b) 3600 rev/kWh  
(c) 1000 rev/kWh                (d) 960 rev/kWh

5. A moving iron ammeter produces a full scale torque of  $240\mu\text{Nm}$  with a deflection of  $120^\circ$  at a current of 10 A. The rate of change of self induction ( $\mu\text{H}/\text{radian}$ ) of the instrument at full scale is

[GATE - 2004]

- (a)  $2.0\mu\text{H}/\text{radian}$                 (b)  $4,8\mu\text{H}/\text{radian}$   
(c)  $12.0\mu\text{H}/\text{radian}$             (d)  $114.6\mu\text{H}/\text{radian}$

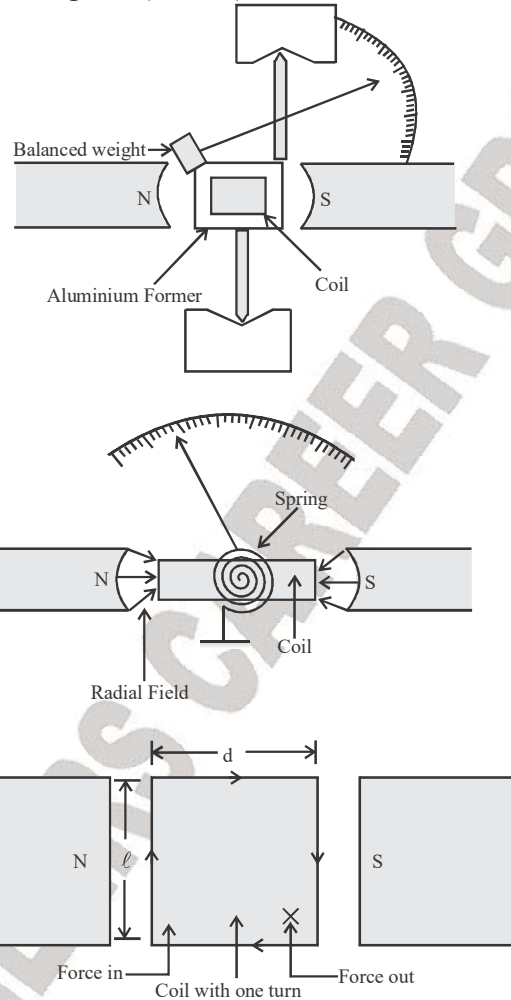**CHAPTER - 5*****ANALOG AMMETER, VOLTMETER AND OHMMETER*****5.1 INTRODUCTION****5.1.1 Permanent Magnet Moving Coil (PMMC)**

$$F = NIBl \sin \theta$$

For radial field;  $\theta = 90^\circ$

$$T_d = F \cdot d$$

$$F = NIBl$$

$$\therefore A = ld$$


$$F = NIBA$$

$$\therefore G = NBA$$

# GATE QUESTIONS

1. Three moving iron type voltmeter are connected as shown below. Voltmeter readings are  $V$ ,  $V_1$  and  $V_2$  as indicated. The correct relation among the voltmeter readings is


[GATE - 2013]

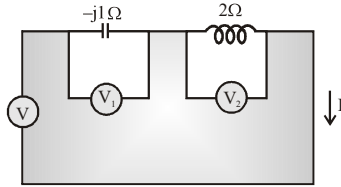

- (a)  $V = \frac{V_1}{\sqrt{2}} + \frac{V_2}{\sqrt{2}}$   
 (b)  $V = V_1 + V_2$   
 (c)  $V = V_1 V_2$   
 (d)  $V = V_2 - V_1$

2. The input impedance of the permanent magnet moving coil (PMMC) voltmeter is infinite. Assuming that the diode shown in the figure below is ideal, the reading of the voltmeter in Volts is


[GATE - 2013]

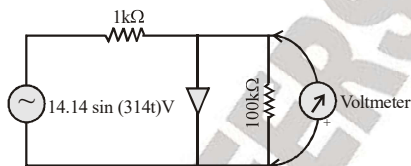

- (a) 4.46  
 (c) 2.23  
 (b) 3.15  
 (d) 0

3. A periodic voltage waveform observed on an oscilloscope across a load is shown. A permanent magnet moving coil (PMMC) meter connected across the same load reads

[GATE - 2012]

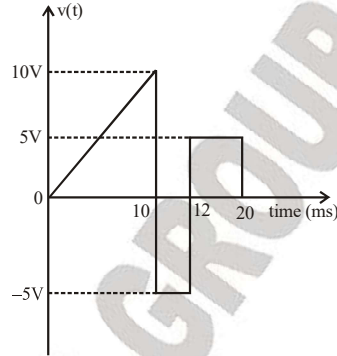

- (a) 4V  
 (c) 8V  
 (b) 5V  
 (d) 10V

4. An analog voltmeter uses external multiplier settings. With a multiplier setting of 20 kΩ, it reads 440V and with a multiplier setting of 80 kΩ, it reads 352V, For a multiplier setting of 40 kΩ, the voltmeter reads

[GATE - 2012]

- (a) 371V  
 (c) 394 V  
 (b) 383V  
 (d) 406V

5. An ammeter has a current range of 0.5 A, and its internal resistance is 0.2 Ω. In order to change the range to 0-25 A, we need to add a resistance of

[GATE - 2010]

- (a) 0.8 Ω in series with the meter  
 (b) 1.0 Ω in series with the meter  
 (c) 0.04 Ω in parallel with the meter  
 (d) 0.05 Ω in parallel with the meter

6. The Q-meter works on the principle of

[GATE - 2005]

- (a) Mutual inductance  
 (c) Series resonance  
 (b) Self inductance  
 (d) Parallel resonance

7. A PMMC voltmeter is connected across a series combination of DC voltage source  $V_1 = 2$  V and AC voltage source  $V_2(t) = 3 \sin(4t)$  V, The meter reads

## ESE OBJ QUESTIONS

1. A  $3\frac{1}{2}$  digit digital voltmeter is accurate to  $\pm 0.5\%$  of reading  $\pm 2$  digits. What is the percentage error, when the voltmeter reads 0.10V on its 10V range?

[EC ESE - 2017]

- (a) 0.025% (b) 0.25%  
(c) 2.05% (d) 20.5%

2. A PMMC instrument if connected directly to measure alternating current, it indicates

[EC ESE - 2017]

- (a) The actual value of the subject AC quantity  
(b) Zero reading  
(c)  $\frac{1}{\sqrt{2}}$  of the scale value where the pointer rests  
(d)  $\frac{\sqrt{3}}{2}$  of the scale value where the pointer rests.

3. Consider the following statements:

Sphere gap method of voltage measurement is used

1. For measuring r.m.s. value of a high voltage
2. For measuring peak value of a high voltage
3. As the standard for calibration purposes

Which of the above statements are correct ?

[EC ESE - 2017]

- (a) 1 and 2 only (b) 2 and 3 only  
(c) 1 and 3 only (d) 1, 2 and 3

4. A voltmeter having a sensitivity of 1000  $\Omega/V$  reads 100 V on its 150 V scale when connected across a resistor of unidentified specifications in series with a milliammeter. When the milliammeter reads 5 mA, the error due to the loading effect of the voltmeter will be nearly

[EC ESE - 2017]

- (a) 13% (b) 18%

(c) 23%

(d) 33%

5. **Statement (I):** Moving iron instruments are used in ac circuits only.

**Statement (II):** The deflecting torque in moving iron instruments depends on the square of the current.

[EE ESE - 2017]

- (a) Both statement (I) and statement (II) are individually true and statement (II) is the correct explanation of statement (I).  
(b) Both statement (I) and statement (II) are individually true but statement (II) is not the correct explanation of statement (I).  
(c) Statement (I) is true but statement (II) is false.  
(d) Statement (I) is false but statement (II) is true.

6. **Statement (I):** PMMC instruments are suitable in aircraft and air space applications.

**Statement (II):** PMMC instruments use a core magnet which possesses self-shielding property.

[EE ESE - 2017]

- (a) Both statement (I) and statement (II) are individually true and statement (II) is the correct explanation of statement (I).  
(b) Both statement (I) and statement (II) are individually true but statement (II) is not the correct explanation of statement (I).  
(c) Statement (I) is true but statement (II) is false.  
(d) Statement (I) is false but statement (II) is true.


7. **Statement (I):** An instrument manufacture as an ammeter should not be used as voltmeter

**Statement (II):** The high resistance winding of an ammeter will suffer serious damage if connected across a high voltage source.

[EE ESE - 2017]


## 6.1 DC CIRCUITS

### 1. Voltmeter – Ammeter method

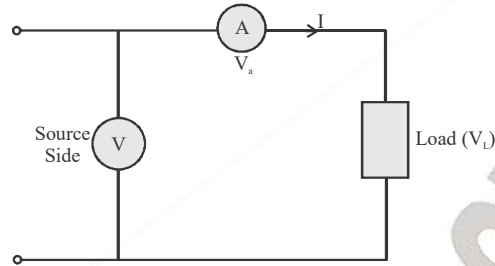

$$\begin{aligned} \text{Power indicated by the instrument is} &= VI \\ &= (V_a + V_L) \cdot I = V_a \cdot I + V_L \cdot I \\ &= V_L I + I^2 R_a \end{aligned}$$

### 2. Actual Power and Loss in Ammeter

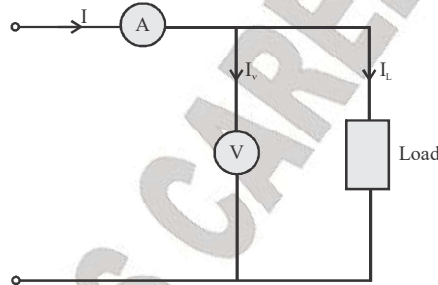

$$\begin{aligned} I &= I_L + I_v \\ \Rightarrow (I_L + I_v)V & \\ \Rightarrow VI_L + I_v V & \\ \Rightarrow VI_L + VI_v & \end{aligned}$$

$$\text{Actual Power and Loss in voltmeter} = V \cdot I_L + \frac{V^2}{R_v}$$

Power indicated by the instrument is actual power and loss in the instrument placed near load.

## 6.2 AC CIRCUITS

Here we use ED type Wattmeter

Fixed coils are connected in series so that they carry load current. Hence fixed coils are also called cc coils (current carrying coils). Moving coil depends on source on load and current carried by moving coils is proportional to voltage. They are also called potential coils or pressure coils.

# GATE QUESTIONS

1. The bridge method commonly used for finding mutual inductance is


[GATE - 2012]

- (a) Heaviside Campbell bridge
- (b) Schering bridge
- (c) De Sauty bridge
- (d) Wien bridge

2. For the circuit shown in the figure, the voltage and current expressions are  $V(t) = E_1 \sin(\omega t) + E_3 \sin(3\omega t)$  and  $i(t) = I_1 \sin(\omega t - \phi_1) + I_3 \sin(3\omega t - \phi_3) + I_5 \sin(5\omega t)$

The average power measured by the wattmeter is


[GATE - 2012]

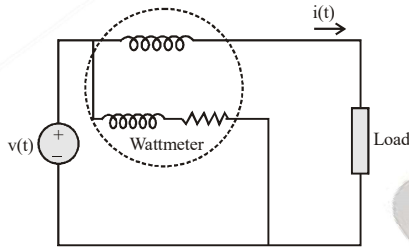

- (a)  $\frac{1}{2} E_1 I_1 \cos \phi_1$
- (b)  $\frac{1}{2} [E_1 I_1 \cos \phi_1 + E_1 I_3 \cos \phi_3 + E_1 I_5]$
- (c)  $\frac{1}{2} [E_1 I_1 \cos \phi_1 + E_3 I_3 \cos \phi_3]$
- (d)  $\frac{1}{2} [E_1 I_1 \cos \phi_1 + E_3 I_1 \cos \phi_1]$

3. A wattmeter is connected as shown in figure. The wattmeter reads.

[GATE - 2010]

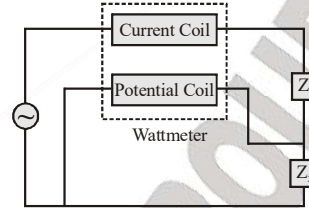

- (a) Zero always
- (b) Total power consumed by  $Z_1$  and  $Z_2$
- (c) Power consumed by  $Z_1$
- (d) Power consumed by  $Z_2$


4. The pressure coil of dynamometer type wattmeter is

[GATE - 2009]

- (a) Highly inductive
- (b) Highly resistive
- (c) Purely resistive
- (d) Purely inductive

5. The figure shows a three-phase delta connected load, supplied from a 400V, 50 Hz, 3-phase balanced source. The pressure coil (PC) and current coil (CC) of a wattmeter are connected to the load as shown, with the coil polarities suitably selected to ensure a positive deflection. The wattmeter reading will be

[GATE - 2009]

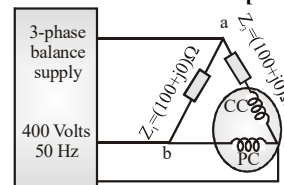

- (a) 0
- (b) 1600 Watt
- (c) 800 Watt
- (d) 400 Watt

6. A sampling wattmeter (that computes power from simultaneously sampled values of voltage and current) is used to measure the average power of a load. The peak to peak voltage of the square wave is 10 V and the current is a triangular wave of 5 A p-p as shown in the figure. The period is 20 ms. The reading in W will be




**CHAPTER - 7****MEASUREMENT OF RESISTANCE****7.1 THREE CATEGORY FOR MEASUREMENT OF RESISTANCE**

- (i) Low R: of order of  $1\Omega$  or less
- (ii) Medium R: of order of  $1\Omega - 100\text{ k}\Omega$
- (iii) High R:  $R > 100\text{ k}\Omega$

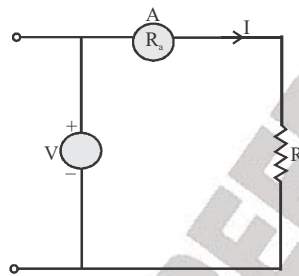**7.2 METHOD TO CALCULATE RESISTANCE****Type-I. Ammeter Voltmeter Method**

This method is suitable for measuring high resistance




$$\text{Measured value of } R_m = \frac{V}{I}$$

$$\text{If } R_a \text{ then, } R_m = \frac{V}{I} = \frac{I R + R_a}{I} = R + R_a$$

$$\text{Percentage error} = \frac{R_a}{R}$$

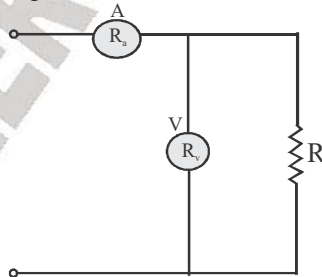**Type-II.**

This method is suitable for measuring low resistances.



$$R_m = \frac{V}{I} = \frac{V}{I_v + I_R}$$

$$I_v = \frac{V}{R_v} \text{ and } I_R = \frac{V}{R}$$



## CHAPTER - 8

### AC BRIDGES

#### 8.1 INTRODUCTION

AC bridges are used for measurement of inductance, capacities, quality factor of coils and dissipation factor of capacitances etc.

Source is an electronic oscillator with controllable frequencies.


##### 1. Detectors are

1. Headphones: 250Hz to 4 kHz
2. Vibration galvanometer: This is most sensitive for 5Hz to 200 Hz.
3. Wide frequency range, tunable amplifier: 100Hz to 10 kHz

At balance,  $\bar{z}_1 \bar{z}_4 = \bar{z}_2 \bar{z}_3$

$$|z_1 \parallel z_4| = |z_2 \parallel z_3| \quad \dots(i)$$

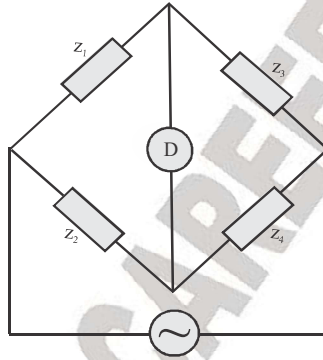
$$\angle\theta_1 + \theta_4 = \angle\theta_2 + \theta_3$$



Two equations: two unknown variable can be known in terms of known variable. For quick balance, the known variables shall not come in the equation.

$$(R_1 + j\omega L_1)R_4 = (R_2 + j\omega L_2)R_3$$

$$R_1 R_4 = R_2 R_3$$

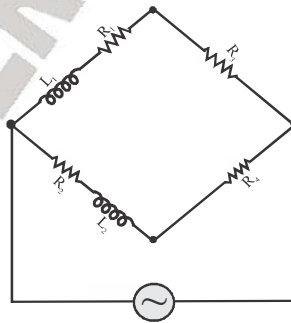

$$\text{And } L_1 R_4 = L_2 R_3$$

$$R_1 = \frac{R_2 R_3}{R_4}$$

# GATE QUESTIONS

1. Consider the following statement


(1) The compensating coil of a low power factor wattmeter compensates the effect of the impedance of the current coil.

(2) The compensating coil of a low power factor wattmeter compensates the effect of the impedance of the voltage coil circuit.

[GATE - 2011]

- (a) (1) is true but (2) is false  
 (b) (1) is false but (2) is true  
 (c) Both (1) and (2) are true  
 (d) Both (1) and (2) are false

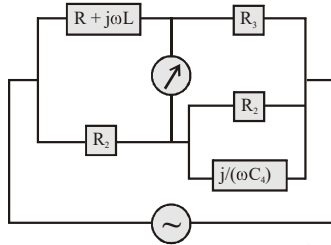
2. The Maxwell's bridge shown in the figure is at balance. The parameters of the inductive coil are.



[GATE - 2010]

- (a)  $R = R_2R_3/R_4$ ,  $L = C_4R_2R_3$   
 (b)  $L = R_2R_3/R_4$ ,  $R = C_4R_2R_3$   
 (c)  $R = R_4/R_2R_3$ ,  $L = 1/(C_4R_2R_3)$   
 (d)  $L = R_4/R_2R_3$ ,  $R = 1/(C_4R_2R_3)$

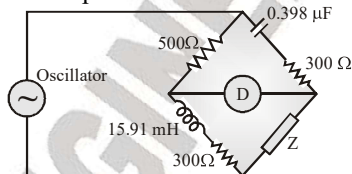3. The ac bridge shown in the figure is used to measure the impedance  $Z$ .




If the bridge is balanced for oscillator frequency  $f = 2$  kHz, then the impedance  $Z$  will be

[GATE - 2008]

- (a)  $(260 + j0)\Omega$                       (b)  $(0 + j200)\Omega$   
 (c)  $(260 - j200)\Omega$                     (d)  $(260 + j200)\Omega$

4. A bridge circuit is shown in the figure below. Which one of the sequence given below is most suitable for balancing the bridge?

[GATE - 2007]

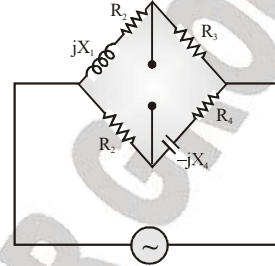

- (a) First adjust  $R_1$                       (b) First adjust  $R_3$   
 (c) First adjust  $R_2$                       (d) First adjust  $R_4$

5.  $R_1$  and  $R_4$  are the opposite arms of a Wheatstone bridge as are  $R_2$  and  $R_3$ . The source voltage is applied across  $R_1$  and  $R_3$ . Under balanced conditions which one of the following is true

[GATE - 2006]

- (a)  $R_1 = R_3R_4/R_2$   
 (b)  $R_1 = R_2R_3/R_4$   
 (c)  $R_1 = R_2R_4/R_3$   
 (d)  $R_1 = R_2 + R_3 + R_4$

6. The items in Group-I represent the various types of measurements to be made with a reasonable accuracy using a suitable bridge. The items in Group-II represent the various bridges available for this purpose. Select the correct choice of the item in Group-II for the corresponding item in Group-I from the following

**List-I**

- A. Resistance in the milli-ohm range  
 B. Low values of Capacitance  
 C. Comparison of resistance which are nearly equal  
 D. Inductance of a coil with a large time-constant

# SOLUTIONS

**Sol. 1. (c)**

The compensation coil compensation the effect of impedance of current coil.

**Sol. 2. (a)**

At balance condition

$$(R + j\omega L) \left( R_4 \parallel \frac{-j}{\omega C_4} \right) = R_2 R_3$$

$$(R + j\omega L) \frac{\frac{-jR_4}{\omega C_4}}{\left( R_4 - \frac{j}{\omega C_4} \right)} = R_2 R_3$$

$$\frac{-jRR_4}{\omega C_4} + \frac{\omega LR_4}{\omega C_4} = R_2 R_3 R_4 - \frac{jR_2 R_3}{\omega C_4}$$

Comparing real & imaginary parts.

$$\frac{RR_4}{\omega C_4} = \frac{R_2 R_3}{\omega C_4}$$

$$R = \frac{R_2 R_3}{R_4}$$

$$\text{Similarly, } \frac{LR_4}{C_4} = R_2 R_3 R_4$$

$$L = R_2 R_3 C_4$$

**Sol. 3. (a)**

Impedance of different branches is given as

$$Z_{AB} = 500\Omega$$

$$Z_{BC} = \frac{1}{j \times 2\pi \times 2 \times 10^3 \times 0.398\mu\text{F}} + 300\Omega$$

$$\square (-200j + 300)\Omega$$

$$Z_{AD} = j \times 2\pi \times 2 \times 10^3 \times 15.91 \text{ mH} + 300\Omega$$

$$\square (200j + 300)\Omega$$

To balance the bridge

$$Z_{AB}Z_{CD} = Z_{AD}Z_{BC}$$

$$500Z = (200j + 300)(9 - 200j + 300)$$

$$500Z = 130000$$

$$Z = (260 + j0)\Omega$$

**Sol. 4. (a)**

To balance the bridge

$$(R_1 + jX_1)(R_4 - jX_4) = R_2 R_3$$


$$(R_1 R_4 + X_1 X_4) + j(X_1 R_4 - R_1 X_4) = R_2 R_3$$

Comparing real and imaginary parts on both sides of equations

$$R_1 R_4 + X_1 X_4 = R_2 R_3 \quad \dots (i)$$

$$X_1 R_4 - R_1 X_4 = 0 \Rightarrow \frac{X_1}{X_4} = \frac{R_1}{R_4} \quad \dots (ii)$$

From eq(1) and (2) it is clear that for balancing the bridge first balance  $R_4$  and then  $R_1$ .

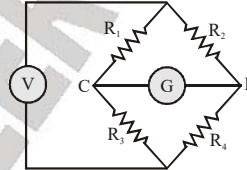**Sol. 5. (b)**

In balanced condition there is no current in CD arm so  $V_C = V_D$

Writing node equation at C and D

$$\frac{V_C - V}{R_1} + \frac{V_C}{R_3} = 0 \Rightarrow V_C = V \left( \frac{R_3}{R_1 + R_3} \right)$$

$$\frac{V_0 - V}{R_2} + \frac{V_D}{R_4} = 0 \Rightarrow V_D = V \left( \frac{R_4}{R_2 + R_4} \right)$$

$$\text{So } V \left( \frac{R_3}{R_1 + R_3} \right) = V \left( \frac{R_4}{R_2 + R_4} \right)$$

$$R_2 R_3 + R_3 R_4 = R_1 R_4 + R_3 R_4$$

$$R_1 = R_2 R_3 / R_4$$

**Sol. 6. (a)**

Kelvin Double bridge is used for measuring low values of resistances. (P → 2)

Low values of capacitances is precisely measured by Schering bridge (Q → 3)


Inductance of a coil with large time constant or high quality factor is measured by hay's bridge (R → 5)

## CHAPTER - 9

## ELECTRONIC MEASUREMENTS

## 9.1 ELECTRONIC MEASUREMENT

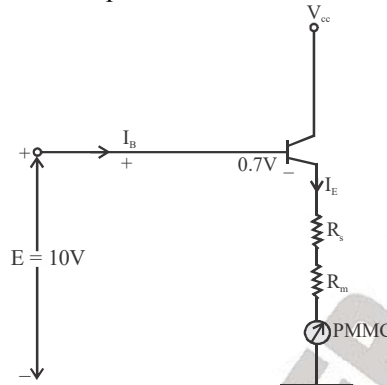**Example** Find  $I_m$  when  $E = 10V$ . Find input resistance with and without transistor.



$$R_s + R_m = 9.3 \text{ k}\Omega$$

$$I_{fsd} = 1 \text{ mA}$$

$$\beta = 100$$

**Solution.**

$$E = 10V = V$$

$$I_m = I_m A$$

$$10 - 0.7 = (9.3 \times 10^3) I_m$$

$$I_m = 1 \text{ mA}$$


$$Z_{in} = (h_{fe} + 1)R_e.$$

$$Z_{in} = \frac{E}{I_B} \Rightarrow Z_{in} = \frac{10}{0.1 \mu A} = 100 \text{ M}\Omega$$

$$I_B \square \frac{I_E}{\beta} = 0.1 \mu A$$

$$Z_{in} = R_s + R_m = R_E$$

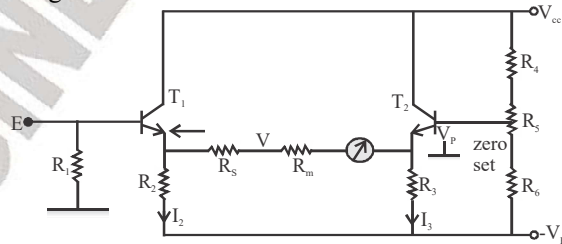Input impedance should be high to avoid loading effect. Thus, to eliminate the error due to  $V_{BE}$ , we will make certain arrangements.



No two transistors can be same.

## GATE QUESTIONS

1. An average-reading digital multi-meter reads 10 V when fed with a triangular wave, symmetric about the time-axis. For the same input an rms reading meter will read


[GATE - 2009]

- (a)  $\frac{20}{\sqrt{3}}$                       (b)  $\frac{10}{\sqrt{3}}$   
 (c)  $20\sqrt{3}$                       (d)  $10\sqrt{3}$

2. The simplified block diagram of a 10-bit A/D converter of dual slope Integrator type is shown in figure. The 10-bit counter at the output is clocked by a 1 MHz clock. Assuming

negligible timing overhead for the control logic, the maximum frequency of the analog signal that can be converted using this A/D converter is approximately

[GATE - 2003]

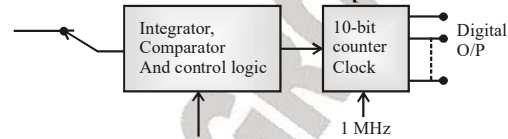

- (a) 2 kHz                      (b) 1 kHz  
 (c) 500 Hz                      (d) 250 Hz

## SOLUTIONS

**Sol. 1. (d)**

Average value of a triangular wave

$$V_{av} = \frac{V_m}{3}$$

$$\text{rms value } V_{ms} = \frac{V_m}{\sqrt{3}}$$

$$\text{Given that } V_{av} = \frac{V_m}{3} = 10V$$

$$\text{So } V_{ms} = \frac{V_m}{\sqrt{3}} = \sqrt{3} V_{av} = 10\sqrt{3} V$$

**Sol. 2. (b)**

Maximum frequency of input in dual slope A/D converter is given as

$$T_m = 2^n T_c$$

Where  $f_m = \frac{1}{T_m} \rightarrow$  maximum frequency of input


$$f_c = \frac{1}{T_c} \rightarrow \text{clock frequency}$$

$$\text{So } f_m = \frac{f_c}{2^n}, \quad n = 10$$

$$= \frac{10^6}{1024} = 1\text{kHz (approx)}$$

**CHAPTER - 10****CATHODE RAY OSCILLOSCOPE (CRO)****10.1 INTRODUCTION**

Cathode Ray Oscillator is basically a XY plotter, the CRO can measure frequency upto 1GHz. CRO is basically voltage meter.

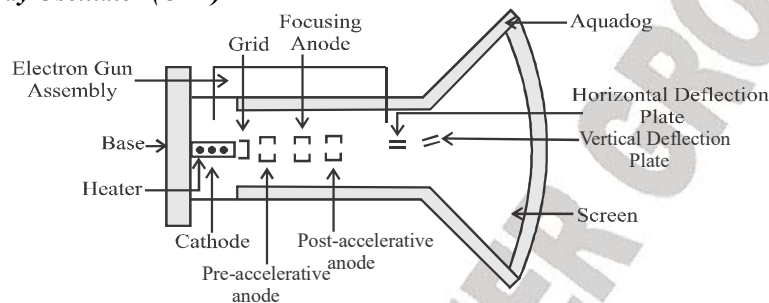**10.1.1 Part of CRO****1. Cathode Ray Oscillator (CRT)**


Electron gun assembly produces sharp beam of accelerated electrons.

- (i) **Cathode:** It produces electrons when heated. A layer of strontium oxide is placed over cathode to increase efficiency. Cathode is cylindrical with a hole in it.
- (ii) **Grid:** The intensity/ brightness spots on screen depends on no. of electrons. This can be controlled by putting a negative bias on grid.
- (iii) **Pre – Accelerative Anode:** By placing positive high voltage, speed of electron increases.
- (iv) **Focusing Anode:** The scattered beam is focused by electrostatic focusing in CRO and by magnetic focusing in TV sets.
- (v) **Post –Accelerative Anode:** It is required to accelerate the electrons.
- (vi) **Horizontal Deflection Plate :** Its function is to move electrons beam horizontally on the screen.
- (vii) **Vertical Deflection Plate:** Its function is to move electrons beam vertically on the screen.
- (viii) **Screen:** It is made of glass coated with phosphor. When electrons strike on phosphor, the energy is increased and it produces light that is called cathode luminance.
- (ix) **Gratiule:** Horizontal and vertical divisions on screen for measurement.
- (x) **Aquadog:** When electrons strike over screen, they cause emission of electrons from screw which is called secondary emission. Aquadog is aqueous summation of device which collect through secondary emitted electrons.

## CHAPTER - 11


### INSTRUMENT TRANSFORMERS

#### 11.1 INTRODUCTION

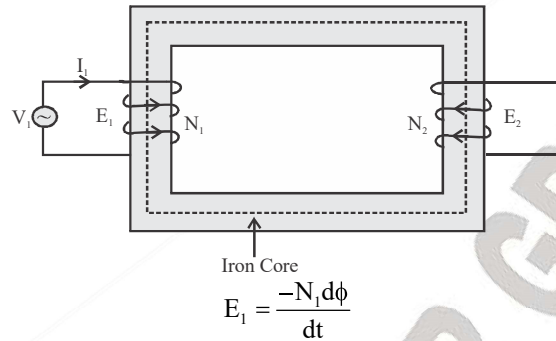

$$E_2 = -N_2 \frac{d\phi}{dt}$$
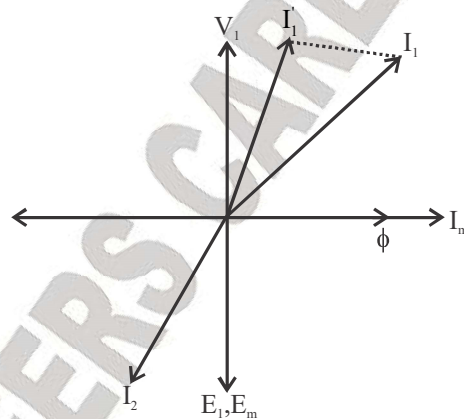
$$\Rightarrow \frac{E_1}{E_2} = \frac{N_1}{N_2}$$



The above graph is phasor diagram of ideal transformer without any load.

If we put some load on transformer, and we get a path for current to flow. So the current produced will be to oppose the flux here,

$$E_1 = 4.44 \phi_m f N_1$$

$$E_2 = 4.44 \phi_m f N_2$$

$$V_1 = -E_1 = 4.44 \phi f N$$

When  $V_1$ ,  $f$  and  $N$  are not changing then even  $\phi$  we cannot change.


$I_2$  causing  $\phi$  decreases. But  $\phi$  cannot on decreasing

Then transformer drives more current from supply to maintain the  $\phi$  such that



## GATE QUESTIONS

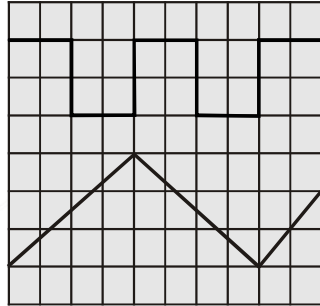1. The time/div and voltage/div axes of an oscilloscope have been erased. A student connects a 1 kHz, 5 V p-p square wave calibration pulse to channel-1 of the scope and observes the screen to be as shown in the upper trace of the figure. An unknown signal is connected to channel-2 (lower trace) of the scope. If the time/div and V/div on both channels are the same, the amplitude (p-p) and period of the unknown signal are respectively



- (a) 5 V, 1 ms  
(c) 7.5 V, 2 ms

- (b) 5 V, 2 ms  
(d) 10 V, 1 ms

[GATE - 2006]

2. 200/1 Current transformer (CT) is wound with 200 turns on the secondary on a toroidal core. When it carries a current of 160 A on the primary, the ratio and phase errors of the CT are found to be  $-0.5\%$  and 30 minutes respectively. If the number of secondary turns is reduced by 1 new ratio-error(%) and phase error(min) will be respectively

- (a) 0.0, 30  
(c) -1.0, 30
- (b) -0.5, 35  
(d) -1.0, 25

[GATE - 2006]

3. A 50 Hz, bar primary CT has a secondary with 500 turns. The secondary supplies 5 A current into a purely resistive burden of  $1 \Omega$ . The magnetizing ampere-turns is 200. The phase angle between the primary and second current is

- (a)  $4.6^\circ$   
(c)  $94.6^\circ$
- (b)  $85.4^\circ$   
(d)  $175.4^\circ$

[GATE - 2004]



**CHAPTER-12****PRIMARY SENSING ELEMENTS AND TRANSDUCERS****12.1 INTRODUCTION**

TYPE	OPERATION
Contacting spindle, pin or figure	displacement to displacement
Proving ring	Force to displacement
Bourdon tube	Pressure to displacement
Bellows	Pressure to displacement
Diaphragm	Pressure to displacement
Spring	Force to displacement
Siesmic mass	Forcing function to displacement
Pendulum scale	Force to displacement
Monometer	Pressure to displacement
Thermocouple	Temperature to electric current
Bi-metallic strip	Temperature to displacement
Temp – stick	Temperature to phase
Float	Fluid level to displacement
Hydrometer	Specific gravity to displacement
Quefis	Fluid velocity to pressure
Venturi tube	Fluid velocity to pressure
Pitot tube	Fluid velocity to pressure
Vanes	Fluid velocity to force


**12.2 CLASSIFICATION OF TRANSDUCERS****1. Principle of Transduction used****(i) Resistive Transducers**

Transducer	Operation	Typical Use
(a) Potentiometer device	Positioning of slider changes the resistance	Measurement of displacement and pressure
(b) Strain Gauge	Resistance of conductors and semi – conductor changes by tensile or compressive stress.	Force, troque, displacement
(c) Pirani Gauge	Resistance of heating element is changed by connection cooling	Gas flow, gas pressure
(d) Thermometer	Resistance changes with temperature with positive $\alpha$ .	Temperature
(e) Thermistor	Resistance changes with temperature with negative $\alpha$ .	Temperature, gas flow, water flow
(f) Photoconductive Cell	Resistance changes by light	Photosensitive relay

**(ii) Capacitive Transducers**

## GATE QUESTIONS

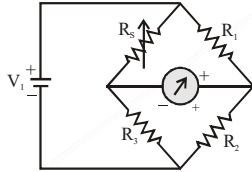1. A strain gauge forms one arm of the bridge shown in the figure below and has a nominal resistance without any load as  $R_s = 300 \Omega$ . Other bridge resistances are  $R_1 = R_2 = R_3 = 300 \Omega$ . The maximum permissible current through the strain gauge is 20mA, During certain measurement when the bridge is excited by maximum permissible voltage and the strain gauge resistance is increased by 1% over the nominal value, the output voltage  $V_0$  in mV is



[GATE - 2013]

- (a) 56.02  
(c) 29.85

- (b) 40.83  
(d) 10.02

2. A  $4\frac{1}{2}$  digit DMM has the error specification as: 0.2% of reading + 10 counts. If a dc voltage of 100 V is read on its 200 V full scale, the

maximum error that can be expected in the reading is

[GATE - 2011]

- (a)  $\pm 0.1\%$   
(c)  $\pm 0.3\%$

- (b)  $\pm 0.2\%$   
(d)  $\pm 0.4\%$

3. Two 8-bit ADCs, one of single slope integrating type and other of successive approximate type, take  $T_A$  and  $T_B$  times to convert 5V analog input signal to equivalent digital output. If the input analog signal is reduced to 2.5 V, the approximate time taken by the two ADCs will respectively, be

[GATE - 2008]

- (a)  $T_A \cdot T_B$   
(c)  $T_A, T_B/2$

- (b)  $T_A/2, T_B$   
(d)  $T_A/2, T_B/2$

4. A digital-to-analog converter with a full-scale output voltage of 3.5 V has a resolution close to 14 mV. Its bit size is

[GATE - 2005]

- (a) 4  
(c) 16

- (b) 8  
(d) 32